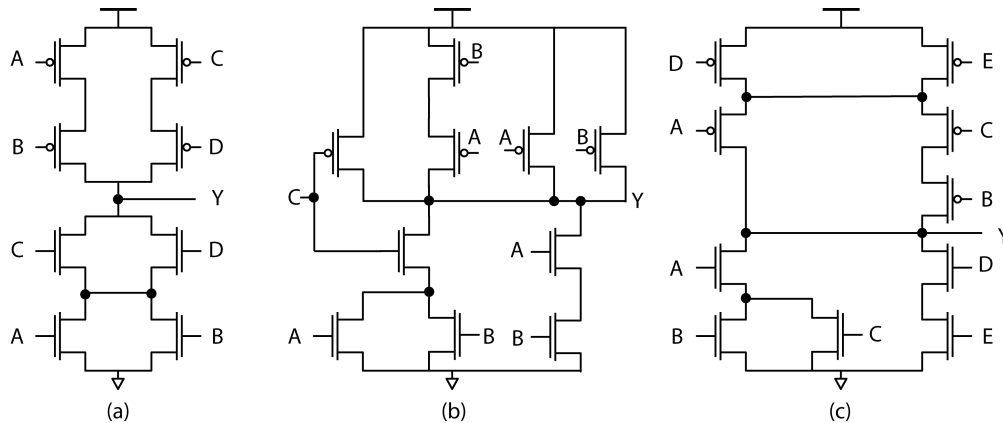


# EECS 151/251A Homework 5

Due 11:59pm Friday, October 15<sup>th</sup>, 2021

## 1 Complementary CMOS

Choose the simplified boolean expression for the function described by the CMOS circuit below.



(a)

- A)  $\overline{(A + B)}(C + D)$
- B)  $\overline{(AB + CD)}$
- C)  $\overline{(AC + DB)}$
- D)  $\overline{(A + C)}(D + B)$

(b)

- A)  $\overline{AB} + \overline{C}(\overline{A} + \overline{B})$
- B)  $\overline{AB + C(A + B)}$
- C)  $\overline{(A + B)}(C + AB)$
- D)  $(A + B)(C + AB)$

(c)

A)  $\overline{A(B + C) + DE}$


B)  $(D + \overline{E})(\overline{A} + \overline{BC})$

C)  $\overline{(D + E)(A + BC)}$

D)  $(\overline{A}(\overline{B} + \overline{C}) + \overline{DE})$

## 2 XOR

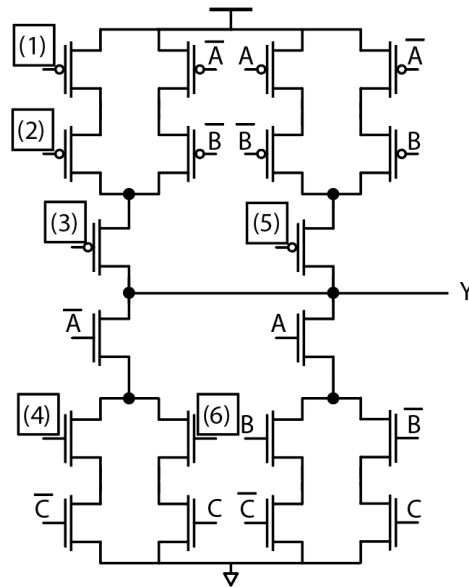(a) Below is a CMOS implementation of a 3-input XOR gate. Complete the circuit by filling in the signal name in the boxes.



1	2	3	4	5	6
---	---	---	---	---	---

- A) 

A	B	C	$\bar{B}$	$\bar{C}$	B
---	---	---	-----------	-----------	---
- B) 

A	B	$\bar{C}$	$\bar{B}$	C	B
---	---	-----------	-----------	---	---
- C) 

A	B	C	B	$\bar{C}$	$\bar{B}$
---	---	---	---	-----------	-----------
- D) 


A	B	$\bar{C}$	B	C	$\bar{B}$
---	---	-----------	---	---	-----------

--

(b) Is the gate shown above a complementary CMOS gate?

--

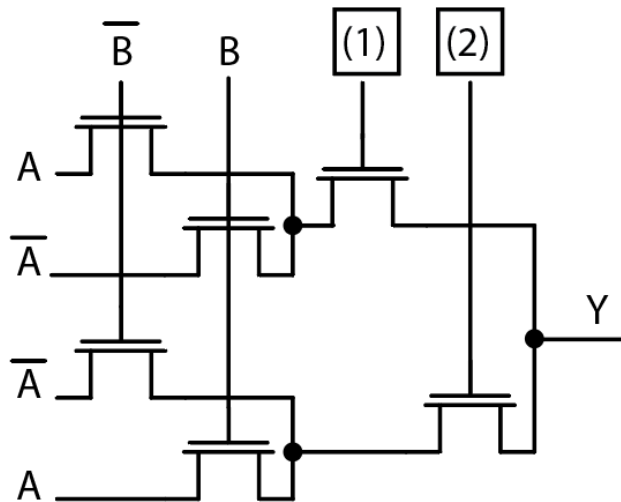(c) Below is a passgate logic implementation of a 3 input XOR gate. Choose the signals that connect to the second stage NMOS gates.



1	2
---	---

A) 

C	$\overline{C}$
---	----------------

B) 

$\overline{C}$	C
----------------	---

C) 

C	C
---	---


D) 

$\overline{C}$	$\overline{C}$
----------------	----------------

--

### 3 Voltage Transfer Characteristic (VTC)

Using the transistor-as-a-switch model, write transition points in the voltage transfer characteristic for the circuit below. You will eventually recognize this as half of a 6T CMOS SRAM bit-cell. Assume that  $|V_{th,p}| = V_{th,n} = V_{DD}/4$  and that  $R_{on,p} = R_{on,n}$ . For example, if the transition point is  $(\frac{1}{2}V_{dd}, \frac{1}{3}V_{dd})$ , write  $\frac{1}{2}, \frac{1}{3}$  in the boxes. If there is only one or two transition points in the middle of the VTC, write 0,0 in the boxes.

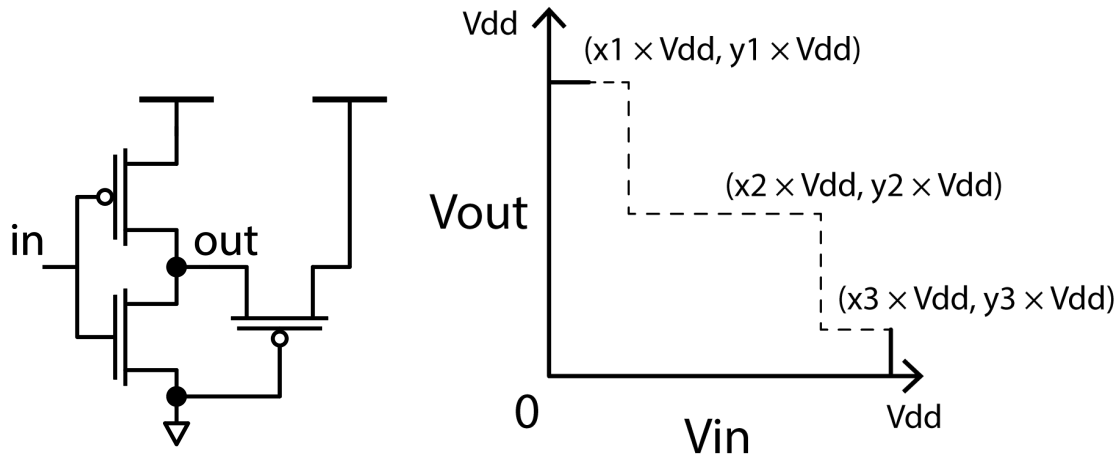

$(x1, y1)$

--	--

$(x2, y2)$

--	--

$(x3, y3)$

--	--