

inst.eecs.berkeley.edu/~eecs151

EECS151 : Introduction to Digital Design and ICs

Lecture 19 – Multipliers, Shifters


Bora Nikolić



Space Jam: Efforts Launched to Corral Orbital Junk

October 28, 2021, EETimes - The quickening pace of satellite launches into low-earth orbit for applications such as global internet coverage is creating a growing space congestion and debris problem. Satellite operators are now required to include additional propellant to de-orbit satellites once their lifetime expires.

 Still, decades-worth of upper stages used to push payloads to intended orbits continue to coast through the solar system. In one recent example, the expended third stage of the Apollo Saturn V—most likely from Apollo 12 launched in October 1969—showed up near Earth in its endless heliocentric orbit.



EECS151 L19 MULTIPLIERS

Nikolić Fall 2021



1

Review

• Adders

- Carry is in the adder critical path
- Mirror adders cells are commonly found in libraries
- Ripple-carry adder is the least complex, lowest energy
- Carry-bypass, carry-select are usually faster than ripple-carry for bitwidths > 8

• Multipliers

- Shift-and-add is the most compact

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021



2

Administrivia

- Homework 7 due this week
- Homework 8 due next week
 - In scope for midterm
- All labs need to be checked off by this week!
- Projects (ASIC and FPGA) started, first check point this week
- Midterm 2 is on November 4 at 7pm
 - Review session tonight at 7pm

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

3 Berkeley
UNIVERSITY OF CALIFORNIA

3



Multipliers

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

4 Berkeley
UNIVERSITY OF CALIFORNIA

4

“Shift and Add” Multiplier

Signed Multiplication:

Remember for 2's complement numbers MSB has negative weight:

$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
 - a) subtract final partial product
 - b) sign-extend partial products
- Modifications to shift & add circuit:
 - a) adder/subtractor
 - b) sign-extender on P shifter register

Convince yourself

- What's -3×5 ?

$$\begin{array}{r} 1101 \\ \times 0101 \\ \hline \end{array}$$



Unsigned Parallel Multiplier

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


 7 Berkeley
 UNIVERSITY OF CALIFORNIA

7

Parallel (Array) Multiplier

$$\begin{array}{r}
 \begin{array}{cccc}
 & a_3 & a_2 & a_1 & a_0 \\
 * & b_3 & b_2 & b_1 & b_0 \\
 \hline
 & & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 + & & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 + & & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 \\
 + & & a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 \\
 \hline
 p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & p_1 & p_0
 \end{array}
 \end{array}$$

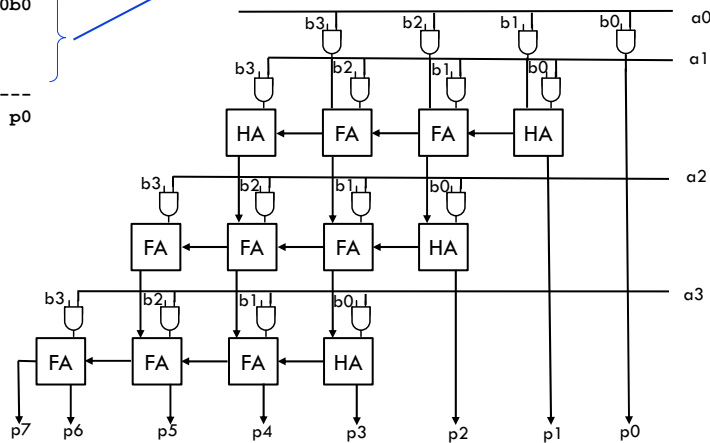multiplicand multiplier
 Partial products, one for each bit in multiplier (each bit needs just one AND gate)



- Performance: What is the critical path?

EECS151 L19 MULTIPLIERS


Nikolić Fall 2021

 8 Berkeley
 UNIVERSITY OF CALIFORNIA

8

Parallel (Array) Multiplier

 Single cycle multiply: Generates all n partial products simultaneously.



EECS151 L19 MULTIPLIERS

Nikolić Fall 2021



9

Carry-Save Addition

- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.

Example: sum three numbers,

$$3_{10} = 0011, 2_{10} = 0010, 3_{10} = 0011$$

$$\begin{array}{r}
 3_{10} \ 0011 \\
 + 2_{10} \ 0010 \\
 \hline
 c \ 0100 = 4_{10} \\
 s \ 0001 = 1_{10}
 \end{array}
 \quad \left. \vphantom{\begin{array}{r} 3_{10} \ 0011 \\ + 2_{10} \ 0010 \\ \hline c \ 0100 = 4_{10} \\ s \ 0001 = 1_{10} \end{array}} \right\} \text{carry-save add}$$

$$\begin{array}{r}
 \text{carry-save add} \left\{ \begin{array}{r} + 3_{10} \ 0011 \\ c \ 0010 = 2_{10} \\ s \ 0110 = 6_{10} \end{array} \right. \\
 \text{carry-propagate add} \left\{ \begin{array}{r} 1000 = 8_{10} \end{array} \right.
 \end{array}$$

- In general, carry-save addition takes in 3 numbers and produces 2: “3:2 compressor”.
- Whereas, carry-propagate takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition


EECS151 L19 MULTIPLIERS

Nikolić Fall 2021




10

Carry-Save Circuits

 

 - When adding sets of numbers, carry-save can be used on all but the final sum.
- Standard adder (carry propagate) is used for final sum.
- Carry-save is fast (no carry propagation) and inexpensive (full adders)




EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

11 Berkeley UNIVERSITY OF CALIFORNIA

11

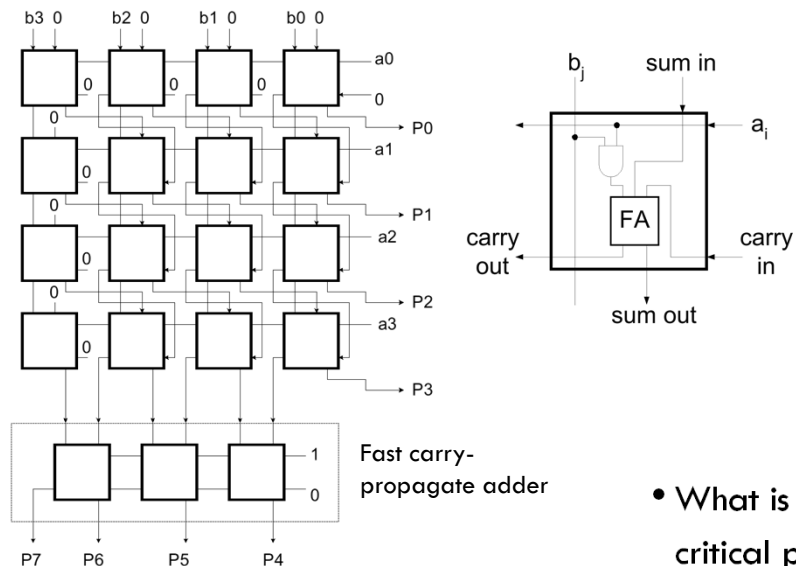Array Multiplier Using Carry-Save Addition



- What is the critical path?

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


12 Berkeley UNIVERSITY OF CALIFORNIA

12

Carry-Save Addition

CSA is associative and commutative. For example:
 
$$(((X_0 + X_1) + X_2) + X_3) = ((X_0 + X_1) + (X_2 + X_3))$$



- A balanced tree can be used to reduce the logic delay
- It doesn't matter where you add the carries and sums, as long as you eventually do add them
- This structure is the basis of the **Wallace Tree Multiplier**
- Partial products are summed with the CSA tree. Fast adder (ex: CLA) is used for final sum
- Multiplier delay $\propto \log_{3/2} N + \log_2 N$

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


13 Berkeley UNIVERSITY OF CALIFORNIA

13


Wallace-Tree Multiplier

- Reduce the partial products in logic stages – 4 x 4 example


Partial products

 


First stage

 

Second stage

 

Final adder

 


EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

14 Berkeley UNIVERSITY OF CALIFORNIA

14

Wallace-Tree Multiplier

 

Note: Wallace tree is often slower than an array multiplier in FPGAs (which have optimized carry chains)

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


15 Berkeley



15

Increasing Throughput: Pipelining

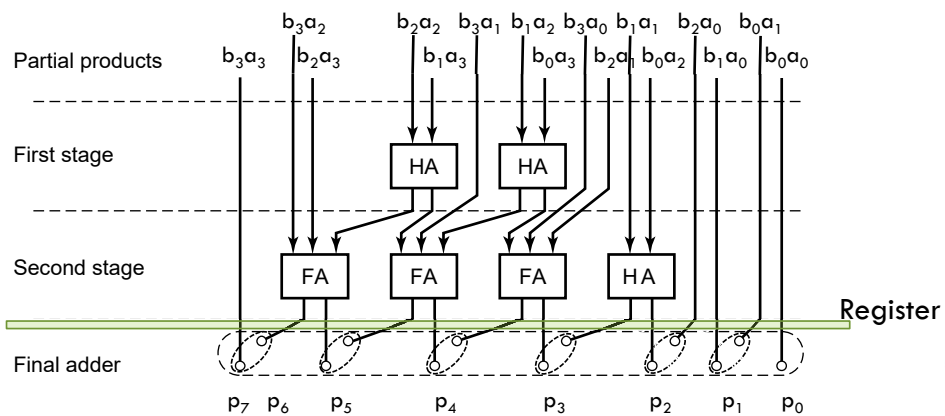- Multipliers have a long critical path: PP generation → reduction tree → final adder
 - Often pipelined before final adder (2x flip-flops for carry-save)



EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

16 Berkeley



16



Booth Recoding

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

17 Berkeley
UNIVERSITY OF CALIFORNIA

17

Booth Recoding: Motivation

$$\begin{array}{rcccc} a_{N-1} \dots & a_2 & a_1 & a_0 & \leftarrow \text{Multiplicand} \\ \times & \underline{b_{N-1} \dots} & b_2 & b_1 & b_0 & \leftarrow \text{Multiplier} \end{array}$$

$$\left. \begin{array}{r} a_{N-1}b_0 \dots a_2b_0 \ a_1b_0 \ a_0b_0 \\ a_{N-1}b_1 \dots a_2b_1 \ a_1b_1 \ a_0b_1 \\ a_{N-1}b_2 \dots a_2b_2 \ a_1b_2 \ a_0b_2 \\ a_{N-1}b_3 \dots a_2b_3 \ a_1b_3 \ a_0b_3 \end{array} \right\} \begin{array}{l} N \text{ partial} \\ \text{products (x } \{0, 1\} \end{array}$$

$$\dots \quad a_1b_0 + a_0b_1 \quad a_0b_0 \leftarrow \text{Product}$$

How many non-zero partial products (out of N)?

- N, if $B = 000\dots 0$
- 0, if $B = 111\dots 1$
- $N/2$ on the average

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

18 Berkeley
UNIVERSITY OF CALIFORNIA

18

Booth Recoding: Main Idea

- Encode ...0111100... patterns:
 - $1111 = 2^3 + 2^2 + 2^1 + 2^0 = 2^4 - 2^0$
 - Only two non-zero numbers, but needs to represent +1 and -1
- Encoding method:
 - Encode pairs of bits, by looking at a window of three bits, from LSB
 - 000 is a middle of string of 0's
 - 001, 011 are the beginnings of a string of 1's
 - 010 is an isolated 1
 - 100, 110 are ends of a string of 1's
 - 101 is the end of one string of 1's and the beginning of the next
 - 111 is the middle of a string of 1's
 - Worst case: ...010101... - exactly a half of non-zero partial products

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


19



19

Booth Recoding: Higher-radix multiplier

 Idea: If we could use, say, 2 bits of the multiplier in generating each partial product we would **halve the number of columns and speed it up!**



Booth's insight: rewrite 2^*A and 3^*A cases, leave $4A$ for next partial product to do!

$$\begin{aligned}
 B_{K+1,K} * A &= 0^*A \rightarrow 0 \\
 &= 1^*A \rightarrow A \\
 &= 2^*A \rightarrow 2A \text{ (or } 4A - 2A) \\
 &= 3^*A \rightarrow 4A - A
 \end{aligned}$$

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

20



20

Booth recoding

(On-the-fly canonical signed digit encoding!)

current bit pair

from previous bit pair

B_{K+1}	B_K	B_{K-1}	action
0	0	0	add 0
0	0	1	add A
0	1	0	add A
0	1	1	add 2*A
1	0	0	sub 2*A
1	0	1	sub A $\leftarrow -2*A+A$
1	1	0	sub A
1	1	1	add 0 \leftarrow

$$\begin{aligned}
 B_{K+1,K} * A &= 0 * A \rightarrow 0 \\
 &= 1 * A \rightarrow A \\
 &= 2 * A \rightarrow 2A \\
 &= 3 * A \rightarrow 4A - A
 \end{aligned}$$

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

21

Berkeley



21


Example

- Compression tree needs to support subtraction

0111	A
x 1010	B

-01110	10 (0) -2A
-00111	101 -A
+0111	001 +A

01000110	

 

A Walther WSR160 arithmometer
(from Wikipedia)

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

22

Berkeley



22

Booth Recoding Notes

- Key advantage: Reduces the number of partial products
 - Compression tree depth becomes $\log_{3/2}[N/2]$
 - Partial product generation is slightly more complex than a NAND2
- Useful for larger multipliers
 - And some very creative solutions for repeated multiplications (FIR filters, etc)



Signed Multipliers


Signed Array Multiplier

- Two's complement

$(-3) * (-2)$

(-3)	(-2)	$\begin{array}{r} 1\ 0\ 1\ (X) \\ * 1\ 1\ 0\ (Y) \\ \hline 0\ 0\ 0\ 0\ 0\ 0 \\ + 1\ 1\ 1\ 0\ 1 \\ - 1\ 1\ 0\ 1 \\ \hline 0\ 0\ 0\ 1\ 1\ 0 \end{array}$	$\begin{array}{l} Y_0 * X = 0 \\ 2Y_1 * X = -6 \\ 4Y_2 * X = -12 \end{array}$
--------	--------	--	---

$(+6)$

 

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

25 Berkeley UNIVERSITY OF CALIFORNIA



25

Combinational Multiplier (signed)

$x_3\ x_2\ x_1\ x_0$	$y_3\ y_2\ y_1\ y_0$

$x_3y_0\ x_3y_1\ x_3y_2\ x_3y_3$	$x_2y_0\ x_2y_1\ x_2y_2\ x_2y_3$
$+ x_1y_0\ x_1y_1\ x_1y_2\ x_1y_3$	$+ x_0y_0\ x_0y_1\ x_0y_2\ x_0y_3$
$- x_3y_3\ x_3y_2\ x_3y_1\ x_3y_0$	$- x_2y_3\ x_2y_2\ x_2y_1\ x_2y_0$

$z_7\ z_6\ z_5\ z_4\ z_3\ z_2\ z_1\ z_0$	

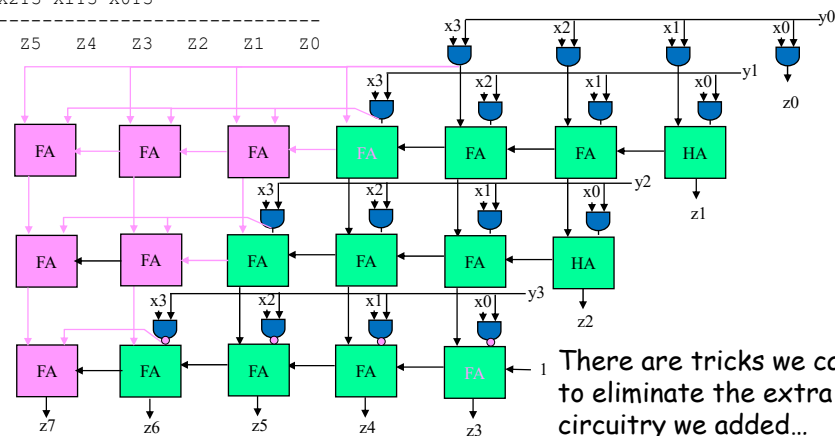 

There are tricks we can use to eliminate the extra circuitry we added...

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

26 Berkeley UNIVERSITY OF CALIFORNIA

26

2's Complement Multiplication (Baugh-Wooley)

Step 1: two's complement operands so high order bit is -2^{N-1} . Must sign extend partial products and **subtract** the last one

$$\begin{array}{r}
 \begin{array}{cccc}
 x_3 & x_2 & x_1 & x_0 \\
 * & y_3 & y_2 & y_1 & y_0 \\
 \hline
 x_3y_0 & x_3y_1 & x_3y_2 & x_3y_3 & x_2y_0 & x_1y_0 & x_0y_0 \\
 + & x_3y_1 & x_3y_2 & x_3y_3 & x_2y_1 & x_1y_1 & x_0y_1 \\
 + & x_3y_2 & x_3y_3 & x_2y_2 & x_1y_2 & x_0y_2 \\
 - & x_3y_3 & x_3y_3 & x_2y_3 & x_1y_3 & x_0y_3 \\
 \hline
 z_7 & z_6 & z_5 & z_4 & z_3 & z_2 & z_1 & z_0
 \end{array}
 \end{array}$$

Step 2: don't want all those extra additions, so add a carefully chosen constant, remembering to subtract it at the end. Convert subtraction into add of (complement + 1).

$$\begin{array}{r}
 \begin{array}{cccc}
 x_3y_0 & x_3y_1 & x_3y_2 & x_3y_3 & x_2y_0 & x_1y_0 & x_0y_0 \\
 + & & & & 1 & & \\
 + & x_3y_1 & x_3y_2 & x_3y_3 & x_2y_1 & x_1y_1 & x_0y_1 \\
 + & & & & 1 & & \\
 + & x_3y_2 & x_3y_3 & x_2y_2 & x_1y_2 & x_0y_2 \\
 + & & & & 1 & & \\
 + & \overline{x_3y_3} & \overline{x_3y_3} & \overline{x_2y_3} & \overline{x_1y_3} & \overline{x_0y_3} & \\
 + & & & & & & 1
 \end{array}
 \end{array}
 \left. \vphantom{\begin{array}{r} \end{array}} \right\} -B = \sim B + 1$$

Step 3: add the ones to the partial products and propagate the carries. All the sign extension bits go away!

$$\begin{array}{r}
 \begin{array}{cccc}
 & \overline{x_3y_0} & x_2y_0 & x_1y_0 & x_0y_0 \\
 + & & \overline{x_3y_1} & x_2y_1 & x_1y_1 & x_0y_1 \\
 + & & \overline{x_2y_2} & x_1y_2 & x_0y_2 \\
 + & \overline{x_3y_3} & x_2y_3 & x_1y_3 & x_0y_3 \\
 + & & & & 1 \\
 - & 1 & 1 & 1 & 1
 \end{array}
 \end{array}$$

Step 4: finish computing the constants...

$$\begin{array}{r}
 \begin{array}{cccc}
 & \overline{x_3y_0} & x_2y_0 & x_1y_0 & x_0y_0 \\
 + & & \overline{x_3y_1} & x_2y_1 & x_1y_1 & x_0y_1 \\
 + & & \overline{x_2y_2} & x_1y_2 & x_0y_2 \\
 + & \overline{x_3y_3} & x_2y_3 & x_1y_3 & x_0y_3 \\
 + & 1 & & & 1 \\
 + & & & & 1
 \end{array}
 \end{array}$$

Result: multiplying 2's complement operands takes just about same amount of hardware as multiplying unsigned operands

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


27

Berkeley



27

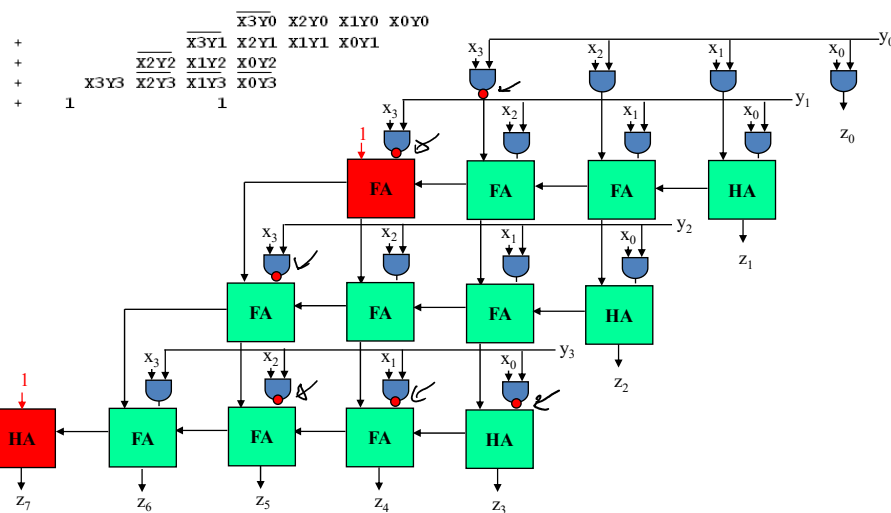2's Complement Multiplication (Baugh-Wooley)



EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

28

Berkeley



28

Multiplication in Verilog

You can use the "*" operator to multiply two numbers:

```
wire [9:0] a,b;
wire [19:0] result = a*b; // unsigned multiplication!
```

If you want Verilog to treat your operands as signed two's complement numbers, add the keyword `signed` to your `wire` or `reg` declaration:

```
wire signed [9:0] a,b;
wire signed [19:0] result = a*b; // signed multiplication!
```

Remember: unlike addition and subtraction, you need different circuitry if your multiplication operands are signed vs. unsigned. Same is true of the `>>>` (arithmetic right shift) operator. To get signed operations all operands must be signed.

```
wire signed [9:0] a;
wire [9:0] b;
wire signed [19:0] result = a*$signed(b);
```

To make a signed constant: `10'sh37C`

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

29

Berkeley
UNIVERSITY OF CALIFORNIA

29



Multiplication with a Constant

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

30

Berkeley
UNIVERSITY OF CALIFORNIA

30


Constant Multiplication

- Our multiplier circuits so far has assumed both the multiplicand (A) and the multiplier (B) can vary at runtime.
- What if one of the two is a constant?

$$Y = C * X$$

- “Constant Coefficient” multiplication comes up often in signal processing. Ex:

$$y_i = \alpha y_{i-1} + x_i$$

 

where α is an application-dependent constant that is hard-wired into the circuit.

- How do we build an array style (combinational) multiplier that takes advantage of a constant operand?

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


31



31

Multiplication by a Constant

 - If the constant C in $C * X$ is a power of 2, then the multiplication is simply a shift of X.
- Ex: $4 * X$



- What about division?
- What about multiplication by non- powers of 2?

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


32




32

Multiplication by a Constant

 - In general, a combination of fixed shifts and addition:
 - Ex: $6 * X = 0110 * X = (2^2 + 2^1) * X = 2^2 X + 2^1 X$



- Details:

 

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


33



33

Multiplication by a Constant

 - Another example: $C = 23_{10} = 010111$



- In general, the number of additions equals one less than the number of 1's in the constant.
- Using carry-save adders (for all but one of these) helps reduce the delay and cost, and using trees helps with delay, but the number of adders is still the number of 1's in C minus 2.
- Is there a way to further reduce the number of adders (and thus the cost and delay)?

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

34



34

Multiplication using Subtraction


- Subtraction is the same cost and delay as addition.
- Consider $C \cdot X$ where C is the constant value $15_{10} = 01111$.
 $C \cdot X$ requires 3 additions.
- We can “recode” 15

$$\text{from } 01111 = (2^3 + 2^2 + 2^1 + 2^0)$$

$$\text{to } 10001 = (2^4 - \bar{2}^0)$$

where $\bar{1}$ means negative weight.

 - Therefore, $15 \cdot X$ can be implemented with only one subtractor.
- Remember Booth encoding



EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

35



35

Canonic Signed Digit Representation

- CSD represents numbers using 1, $\bar{1}$, & 0 with the least possible number of non-zero digits.
 - Strings of 2 or more non-zero digits are replaced with a $1000..\bar{1}$.
 - Leads to a unique representation.
- To form CSD representation might take 2 passes:
 - First pass: replace all occurrences of 2 or more 1's:

$$01..10 \text{ by } 10..\bar{1}0$$

- Second pass: same as above, plus replace $01\bar{1}0$ with 0010 and $0\bar{1}10$ with $00\bar{1}0$
- Examples:

$011101 = 29$	$0010111 = 23$	$0110110 = 54$
$100\bar{1}01 = 32 - 4 + 1$	$001100\bar{1}$	$10\bar{1}10\bar{1}0$
	$010\bar{1}00\bar{1} = 32 - 8 - 1$	$100\bar{1}0\bar{1}0 = 64 - 8 - 2$

- Can we further simplify the multiplier circuits?

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


36



36


(K) Constant Coefficient Multiplication (KCM)

 Binary multiplier: $Y = 231 * X = (2^7 + 2^6 + 2^5 + 2^2 + 2^1 + 2^0) * X$




- CSD helps, but the multipliers are limited to shifts followed by adds.

 • CSD multiplier: $Y = 231 * X = (2^8 - 2^5 + 2^3 - 2^0) * X$



- How about shift/add/shift/add ...?

 • KCM multiplier: $Y = 231 * X = 7 * 33 * X = (2^3 - 2^0) * (2^5 + 2^0) * X$



- No simple algorithm exists to determine the optimal KCM representation.
- Most use exhaustive search method.

<http://www.andraka.com/multipli.php>

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

37

Berkeley UNIVERSITY OF CALIFORNIA



37



Shifters and Rotators

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


38

Berkeley UNIVERSITY OF CALIFORNIA



38

Fixed Shifters / Rotators Defined

 

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


39



39

Variable Shifters / Rotators

 - Example: $X \gg S$, where S is unknown at design time.
- Uses: Shift instruction in processors, floating-point arithmetic, division/multiplication by powers of 2, etc.
- One way to build this is a simple shift-register:
 - a) Load word, b) shift enable for S cycles, c) read word.



- Worst case delay $O(N)$, not good for processor design.
- Can we do it in $O(\log N)$ time and fit it in one cycle?

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021


40



40

Log Shifter / Rotator

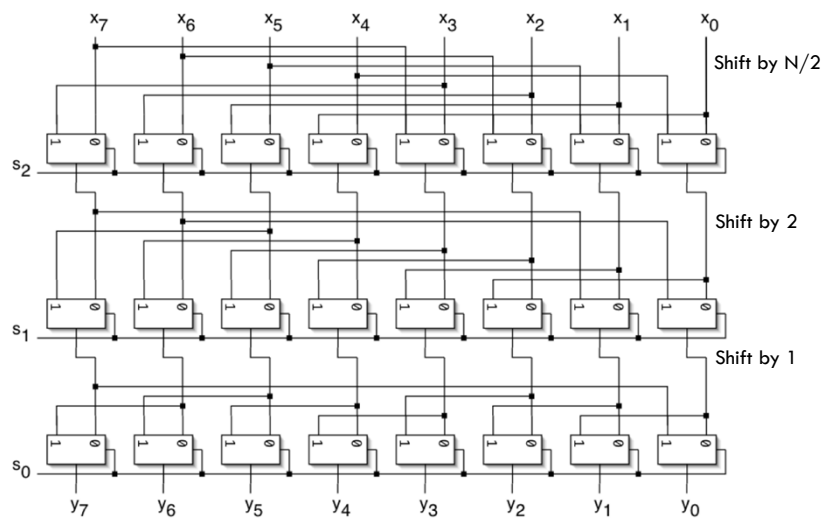- Log(N) stages, each shifts (or not) by a power of 2 places, $S=[s_2;s_1;s_0]$:



EECS151 L19 MULTIPLIERS


Nikolić Fall 2021

41



41



LUT Mapping of Log shifter

 

Efficient with 2-to-1 multiplexers, for instance, 3LUTs.

Virtex6 has 6LUTs. Naturally makes 4-to-1 muxes:

Reorganize shifter to use 4to1 muxes.

  

Final stage uses F7 mux

EECS151 L19 MULTIPLIERS


Nikolić Fall 2021

42



42

“Improved” Shifter / Rotator

 

- Requires careful (custom) circuit design:
 - High fanout on input signals $x_0 \dots x_7$
 - Large multiplexers are slow

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

43


Berkeley



43

Barrel Shifter

 - Cost/delay?
 - (don't forget the decoder)



EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

44


Berkeley



44


Crossbar Switch

 - $N \log(N)$ control signals.
- Supports all interesting permutations
 - All one-to-one and one-to-many connections.
- Processors to memory/peripherals
- Communication hardware (switches, routers).



Western Electric 100-point six-wire Type B crossbar switch (Wikipedia)

EECS151 L19 MULTIPLIERS

 

Nikolić Fall 2021

45

Berkeley



45

Review

- Binary multipliers have three blocks:
 - Partial-product generation (NAND or Booth)
 - Partial-product compression (ripple-carry array, CSA or Wallace)
 - Final adder
- Multipliers are often pipelined
- Constant multipliers can be optimized for size/speed
- Shifters and crossbars are common building blocks in digital systems
 - Often require customization

EECS151 L19 MULTIPLIERS

Nikolić Fall 2021

46

Berkeley



46